

ELEN 20005 FOUNDATIONS OF ELECTRICAL NETWORKS

Semester 2 Exam 2017

Numerical Answers

Question 1

- (a) The clockwise mesh currents are $i_1 = 2 \text{ A}$, $i_2 = -1 \text{ A}$, $i_3 = -0.8 \text{ A}$, $i_4 = -1 \text{ A}$.
(b) $v_1 = -19 \text{ V}$, $v_2 = 4 \text{ V}$.
(c) Absorbing 0.8 W of power. (d) $L = 3.3 \text{ mH} \pm 2\%$ (e) $C = 4.7 \text{ nF}$

Question 2

- (a) $V_C(0^+) = 10 \text{ V}$, $V_C(t) = 10e^{-200t} \text{ V}$. (b) 8 ms .
(c) $w_C(0) = 125 \text{ } \mu\text{J}$, $w_C(t) = 125e^{-400t} \text{ } \mu\text{J}$.

Question 3

- (b) $V_{ab} = 762/30^\circ \text{ V}$, $I_{aA} = 88/-36.9^\circ \text{ A}$ (c) $V_{AB} = 762/30^\circ$, $I_{AB} = 50.8/-6.9^\circ \text{ A}$
(d) $\theta = 36.9^\circ$, $P = 15.5 \text{ kW}$, $Q = 11.6 \text{ kVAR}$.

Question 4

- (a) $V_T = 80/0^\circ \text{ V}$, $Z_T = 41.2/14.1^\circ \Omega$ (b) $\mathbf{V} = 20/-90^\circ \text{ V}$, $v(t) = 20 \cos(1000t - 90^\circ) \text{ V}$.

Question 5

- (a) $A_m = 10 \text{ V}$, $\omega = 500\pi \text{ rad/s}$, $\theta = -90^\circ$. (b) V_2 lags V_1 by 54° .

Question 6

- (b) $i(t) = 3.5 \cos(1000\pi t + 14.5^\circ) \text{ mA}$, $v_C(t) = 0.5 \cos(1000\pi t - 75.5^\circ) \text{ V}$,
phase difference is 75.5°

Question 7

- $i(0) = 1 \text{ mA}$, $i(2) = 2 \text{ mA}$ with quadratic curve inbetween;
 $i(2) = 2 \text{ mA}$, $i(4) = 2 \text{ mA}$ with constant curve inbetween;
 $i(4) = 2 \text{ mA}$, $i(5) = 1 \text{ mA}$ with straight line inbetween.
 $p(0) = 0 \text{ mW}$, $p(2^-) = 30 \text{ mW}$ with cubic curve inbetween;
 $p(2^+) = 0 \text{ mW}$, $p(4^-) = 0 \text{ mW}$ with constant curve inbetween;
 $p(4^+) = -30 \text{ mW}$, $p(5) = -15 \text{ mW}$ with straight line inbetween.
 $w(0) = 7.5 \text{ nJ}$, $w(2) = 30 \text{ nJ}$ with quartic curve inbetween;
 $w(2) = 30 \text{ nJ}$, $w(4) = 30 \text{ nJ}$ with constant curve inbetween;
 $w(4) = 30 \text{ nJ}$, $w(5) = 7.5 \text{ nJ}$ with quadratic curve inbetween.

Question 8

- (a) $Y = \overline{A} \overline{B} + \overline{A} \overline{C}$ (c) False

Question 9

- (a) $Z = \overline{BC} + \overline{B(A+C)}$ (b) $Z(ABC) = 1$, otherwise $Z = 0$.
(c) The worst-case propagation delay goes through the OR gate, the NAND gate and the NOR gate with total $t_{pd} = 58 \text{ ns}$.

Question 10

$$v_{out} = \begin{cases} \frac{1}{3}(v_{IN} + 7 \text{ V}), & \text{if } v_{IN} \geq 14 \text{ V} \\ \frac{1}{2}v_{IN}, & \text{if } v_{IN} < 14 \text{ V} \end{cases}.$$